

# Phy 132 Solutions - HW IVa


Session IV.1

1)



$$\Delta V = IR = .25A \cdot 15\Omega = \boxed{3.75V}$$

2)

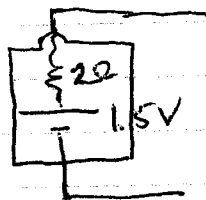


a)




$$I = \frac{\Delta V}{R} = \frac{1.5V}{2\Omega} = \boxed{.75A}$$

b) Compare

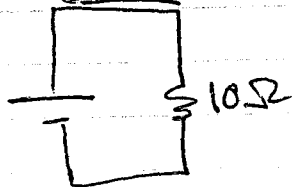

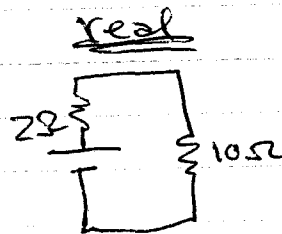
$$I_{\text{ideal}} = \frac{\Delta V}{R} = \frac{1.5V}{10\Omega} = .15A$$



$$I_{\text{real}} = \frac{1.5V}{12\Omega} = .125A$$


real is .025A less than ideal

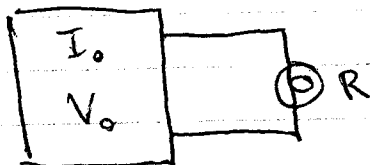3) We will assume (which is not quite correct!) that each bulb acts like a resistor. Let's define  $I_0$  &  $V_0$  as those for a single bulb




$$V_0 = I_0 R$$

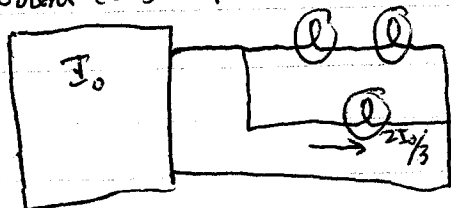const I case  
current const - splits 2:1  $I_0/3$




const V case

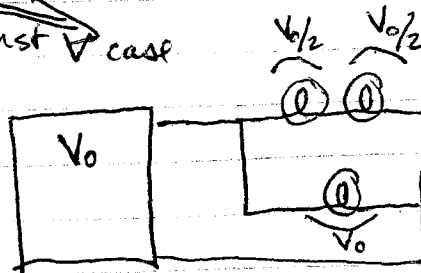

So, we know I's in const V case by  $\Delta V = IR$ , so
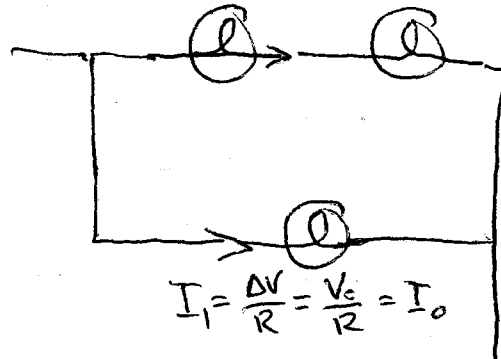
$$I_2 = \frac{\Delta V}{R} = \frac{V_0/2}{R} = I_0/2$$



$$I_1 = \frac{\Delta V}{R} = \frac{V_0}{R} = I_0$$


So, more current flows in the constant voltage case ( $\frac{3}{2}I_0$ ) than in the constant current case ( $I_0$ ). Notice the ratio of currents stays the same:


$$b) \quad \frac{I_1}{I_2} = \frac{I_0}{I_0/2} = \frac{2I_0/3}{I_0/3} = 2$$

const V case
const I case

Session IV.2

1) What is equiv R:

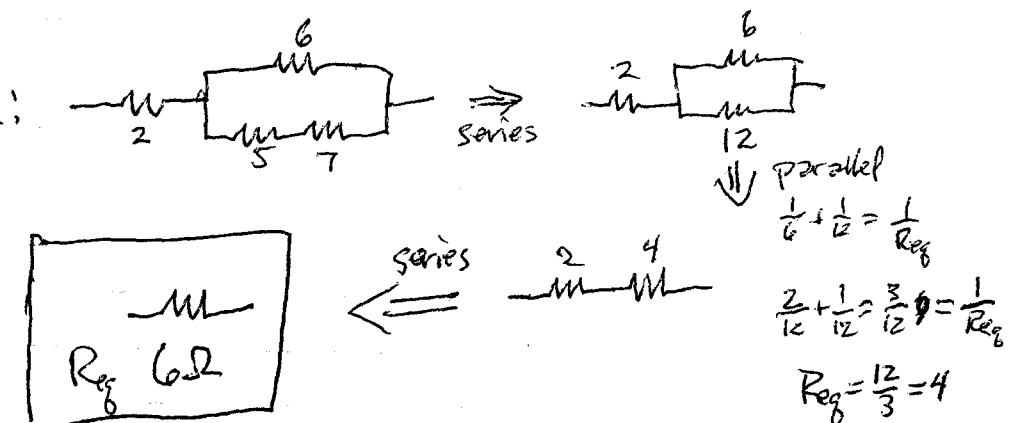

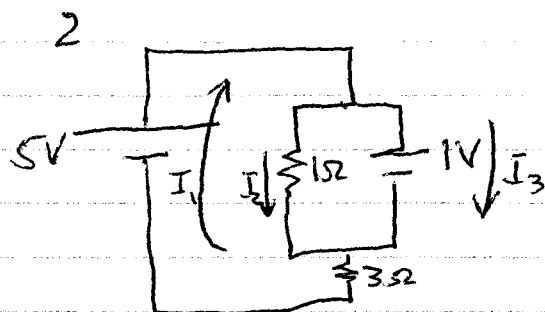

Junctions:  $I_1 = I_2 + I_3$  a)  
 $I_2 + I_3 = I_1$  b)

Loops:  $5V - I_2 1\Omega - I_1 3\Omega = 0$  1)

$5V - 1V - I_1 3\Omega = 0$  2)

$1V - I_2 1\Omega = 0$  3)

Need to find 3 unknowns -  $I_1, I_2, I_3$  - so need 3 eq'ns.

Need to include each circuit element (R or V) somewhere,  
 & include each current in at least 1 jct eqn.

I'll choose equations a), 1), & 2) (which is not the  
 best choice - a), 2), & 3) is easier.

a)  $I_1 = I_2 + I_3$

1)  $5V - I_2 1\Omega - I_1 3\Omega = 0$

2)  $5V - 1V - I_1 3\Omega = 0 \Rightarrow 4V = I_1 3\Omega \Rightarrow \boxed{I_1 = \frac{4}{3} A}$

plug that result into 1) to find


$5V - I_2 1\Omega - \frac{4}{3} A \cdot 3\Omega = 0 = 5V - I_2 1\Omega - 4V = 1V - I_2 1\Omega = 0$

so  $\boxed{I_2 = \frac{1V}{1\Omega} = 1A}$

then plug those two currents  
 into a:

$\frac{4}{3} A = 1A + I_3 \Rightarrow \boxed{I_3 = \frac{1}{3} A}$

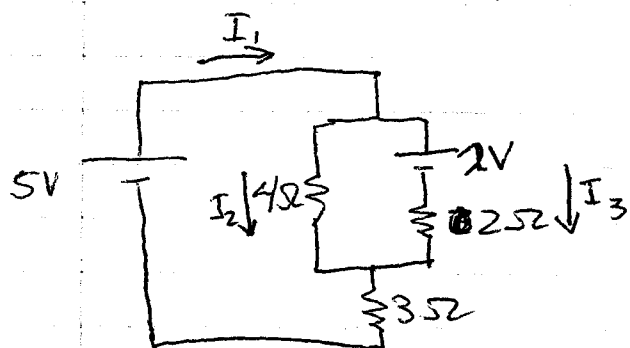Just as an example - what if we had this circuit:



Let:  $I_1 = I_2 + I_3$  a)

loops  $5V - I_2 4\Omega - I_1 3\Omega = 0$  1)

$-2V - I_3 2\Omega + I_2 4\Omega = 0$  2)

Now, not so simple! Choose to move from 3 eq's & 3 unknowns to 2 eq's & 2 unknowns by eliminating one current - say  $I_3$ .

First - combine a) & 2):  $I_3 = I_1 - I_2 \Rightarrow$  plug into 2

~~$-2V - (I_1 - I_2) 2\Omega + I_2 4\Omega = 0$~~

$-2V - I_1 2\Omega + I_2 6\Omega = 0$  3)

~~Eg'n 1)~~ Eg'n 1) never had  $I_3$ , so now we have 2 eq's & 2 unknowns:

$-2V - I_1 2\Omega + I_2 6\Omega = 0$  3)

$5V - I_2 4\Omega - I_1 3\Omega = 0$  1)

Now let's eliminate  $I_2$ . Could solve for  $I_2$  from 3 & substitute into 1, or - multiply 3) by 2:

~~$-4V + I_2 12\Omega - I_1 4\Omega = 0$~~

and 1) mult. by 3:  $15V - I_2 12\Omega - I_1 9\Omega = 0$  and add  
 $11V + 0 - I_1 13\Omega = 0 \Rightarrow \boxed{I_1 = \frac{11}{13} A}$

Plug that into, say 3)

$-2V - \left(\frac{11}{13} A\right) 2\Omega + I_2 6\Omega = 0 \Rightarrow I_2 = \left(2V + \frac{22}{13} V\right) / 6\Omega = \left(\frac{48}{13}\right) / 6 = \boxed{\frac{8}{13} A}$

Then a):  $I_3 = I_1 - I_2 = \frac{11}{13} - \frac{8}{13} = \boxed{\frac{3}{13} A}$