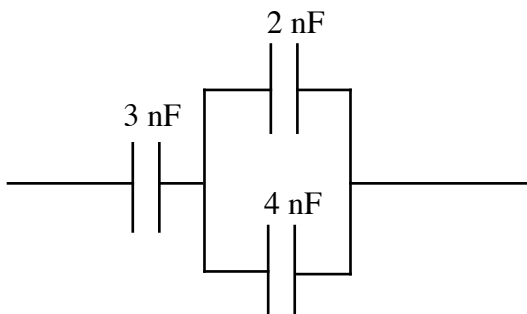


Homework V-VI

Session V.2

1. What is the effective capacitance of the following network of capacitors?



2. For problem 1, imagine that the full network is connected to a 5 V battery.
- Use the equivalent capacitance from problem 1 to find the total charge supplied by the battery.
 - Use charge conservation and $C = Q/\Delta V$ to find the charge on each of the capacitors (that is, the charge on the positive plate of each capacitor).

Session V.3

3. Just as batteries have internal resistances (effectively a resistance in series), so do capacitors--it is just as if the leads to the capacitor are really resistors rather than good conductors. This is particularly true of our green 0.47 F capacitors. You also may have noticed that to discharge them even with a wire, one has to hold the wire in contact with the capacitor for a few seconds. Explain how these effects are related. Then estimate the internal resistance to within a factor of two or three.
4. A 0.005 F capacitor is charged to 8 V. It is then discharged through a 10,000 Ω resistor. How long does it take for the voltage to drop to 2 V?

Session VI.1

5. A 1.5 volt battery is connected in series with a 100 Ω resistor. How much total charge in Coulombs passes through that resistor in one minute?
6. A 0.5 F capacitor is charged to 2 V over 20 seconds. What is the average electrical current flowing?

7. A capacitor of capacitance .04 F is charged by a 1.5 V battery through a resistor $R = 200 \, \Omega$.

a) Estimate the average charging current as $\Delta V/R$. Is this reasonable?

b) How long does it take to charge the capacitor, assuming this current does not change (in reality it does)?

c) Use this method with an arbitrary R , C , and ΔV . Can you get an expression for the charging time in terms of R , C , and ΔV ?

8. Does the charge stored on a capacitor tend to hold the two plates together, or to push them apart? In the process, explain the statement “While we say that a capacitor stores charge, in fact the net charge on the capacitor at all times is actually zero.”