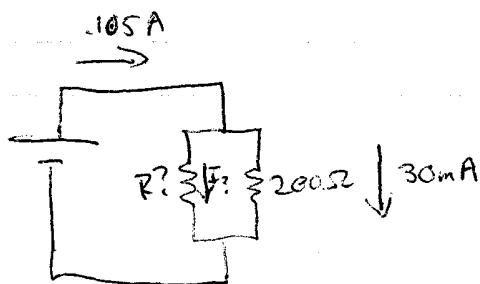


# HW IV-V - Phy 132

Session IV.3

1)



Since  $200\Omega$  &  $R?$  are in parallel, they have the same  $\Delta V = IR$


$$= .03A \cdot 200\Omega = \underline{6V}$$

By junction equation, current through  $R?$ , call it  $I?$ , is given by  $.105A = I? + .03A \Rightarrow I? = .075A$

So,  $R?$  is given by  $V = 6V = I? R? \Rightarrow R? = \frac{6V}{.075A} = \underline{80\Omega}$

(Many other ways to argue this.)

2)

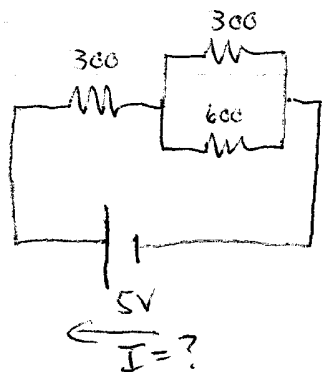


This can be done by equivalent resistors: First 2 in parallel:

$$\frac{1}{R_{\text{par}}} = \frac{1}{300} + \frac{1}{300} = \frac{2}{300} = \frac{1}{150}$$

$$R_{\text{par}} = 150\Omega$$


So, this becomes

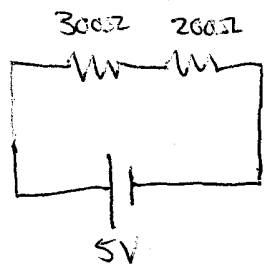

These in series are equivalent to  $450\Omega$ , so  $I = \frac{V}{R} = \frac{5V}{450\Omega}$

$$= \underline{.01A}$$

3) This must be done by Kirchhoff:

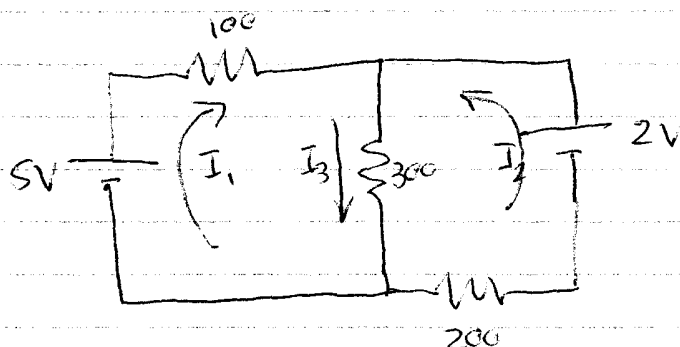

Need 2 loops, 1 junction

$$5V - I_1 \cdot 100\Omega - I_3 \cdot 300\Omega = 0 \quad 1)$$

$$2V - I_3 \cdot 300\Omega - I_2 \cdot 200\Omega = 0 \quad 2)$$

$$I_1 + I_2 = I_3 \quad 3)$$

First, let's eliminate  $I_1$ . Use  $I_1 = I_3 - I_2$ , so, eq'n 1) become

$$5V - (I_3 - I_2) \cdot 100\Omega - I_3 \cdot 300\Omega = 0$$

$$\text{or } 5V + I_2 \cdot 100\Omega - I_3 \cdot 400\Omega = 0 \quad \text{Let's double this:}$$

$$10V + I_2 \cdot 200\Omega - I_3 \cdot 800\Omega = 0 \quad \text{\$ add to 2}$$

$$2V - I_2 \cdot 200\Omega - I_3 \cdot 300\Omega = 0$$

$$12V + 0 - I_3 \cdot 1100\Omega = 0$$

$$I_3 = \frac{12V}{1100\Omega} \approx 1.09 \times 10^{-2} A$$

Now, we plug this into 1):

$$5V - I_1 \cdot 100\Omega - (1.09 \times 10^{-2} A) \cdot 300\Omega = 0$$

$$1.73V - I_1 \cdot 100\Omega = 0 \Rightarrow I_1 = \frac{1.73V}{100\Omega} = .0173A$$

And finally, use 3:  $I_2 = I_3 - I_1 = (1.09 \times 10^{-2} - 1.73 \times 10^{-2}) A$

$$I_2 = -6.4 \times 10^{-3} A$$

## Session V.1

$$1) C = 200 \mu\text{F}, V = 5\text{V} \Rightarrow Q = C \cdot V$$

$$= 2 \times 10^{-4} \text{F} \cdot 5\text{V}$$

$$= 10^{-3} \text{C}$$

To double this, must double  $V$ , since  $Q$  is proportional to  $V$  — so 10V

$$2) C = 2 \times 10^{-3} \text{F} \quad I = 10^{-3} \text{A} = \frac{dQ}{dt}$$

$$Q = \int I dt = I \cdot \Delta t = 10^{-3} \text{A} \cdot 3 \text{sec} = 3 \times 10^{-3} \text{C}$$

↑ since  $I$  constant

After 5 sec,


$$V = \frac{Q}{C} = \frac{10^{-3} \text{A} \cdot 5 \text{sec}}{2 \times 10^{-3} \text{F}} = 2.5 \text{V}$$

After  $t$  sec

$$V = \frac{Q}{C} = \frac{10^{-3} \text{A} \cdot t \text{sec}}{2 \times 10^{-3} \text{F}} = \frac{t}{2} \text{V}$$

3) a) Immediately after connection to  $R$ ,  $C$  is still charged to 4V — no appreciable charge has left yet. So, initial  $I$  is  $V/R = \frac{4\text{V}}{2000\Omega} = 2 \times 10^{-3} \text{A}$ .

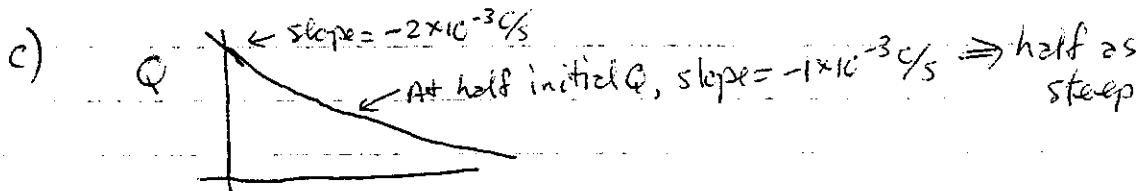b) When  $V = 2\text{V}$ ,  $I = \frac{2\text{V}}{2000\Omega} = 1 \times 10^{-3} \text{A}$



$$4) C_1 = 10^{-3} F = 1 \text{ mF} \quad C_2 = 5 \times 10^{-4} F = 0.5 \text{ mF}$$

$$a) \text{ in parallel, } C_T = C_1 + C_2 = 1.5 \times 10^{-3} F = \boxed{1.5 \text{ mF}}$$

$$b) \text{ in series } \frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{1 \text{ mF}} + \frac{1}{0.5 \text{ mF}} = \frac{3}{1 \text{ mF}}$$

$$C_T = \frac{1}{3} \text{ mF} = \boxed{3.3 \times 10^{-4} F}$$