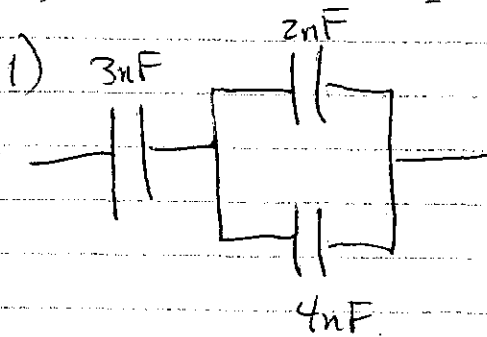


Session Vc 2



$2 \text{ \& } 4$ in parallel
gives 6nF .

This plus 3nF is
series give

$$\frac{1}{C_T} = \frac{1}{3\text{nF}} + \frac{1}{6\text{nF}}$$

$$= \frac{3}{6\text{nF}} = \frac{1}{2\text{nF}}$$

So $C_T = 2\text{nF}$

2) a) Connect above to $5\text{V} \Rightarrow Q = CV = 2\text{nF} \cdot 5\text{V} = 10\text{nC} = 10^{-8}\text{C}$

b) 3nF is in series, so, it is charged to full 10nC


$2 \text{ \& } 4\text{nF}$ share the 10nC . Since they are in parallel, they

have the same $V = \frac{Q}{C}$ so $\frac{Q_2}{C_2} = \frac{Q_4}{C_4}$ so $\frac{Q_2}{Q_4} = \frac{C_2}{C_4} = \frac{1}{2}$. So

$Q_2 = \frac{10}{3}\text{nC}$ & $Q_4 = \frac{20}{3}\text{nC}$ (Ratio of $2:1$ & add to 10nC)

Phy 132 HW V-VI

V.3 3) So, C is like

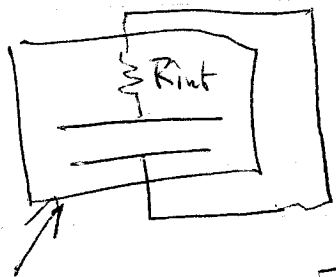

Real Capacitor

← so even discharge like this has a time constant of $R_{int} \cdot C$.

If it takes a few seconds to discharge nearly completely (which must be at least 2-3 lifetimes of $\tau = RC$), then we can guess $RC \approx 1 \text{ sec}$

So if $C = .5 \text{ F}$, then $\boxed{R \approx 2 \Omega}$.

42) $.005 \text{ F}$ to 8 V . Discharge thru $10^4 \Omega$.

$$\text{So } \tau = RC = 50 \text{ sec}$$

Dropping to 2V takes 2 half lives (one to 4V, two to 2V), and we found

$$T_{1/2} = \ln 2 \cdot \tau = 35 \text{ sec}$$

Take $2 \times T_{1/2} = \boxed{70 \text{ sec}}$ to drop from 8V to 2V

VI.1



$$I = \frac{dQ}{dt} = \frac{V}{R} = \frac{1.5 \text{ V}}{100 \Omega} = .015 \text{ A}$$


$$Q = \int \frac{dQ}{dt} dt = \underset{\substack{\uparrow \\ \text{const } I}}{I} t = .015 \text{ A} \cdot 60 \text{ sec} = \boxed{0.9 \text{ C}}$$

64) .5F charged to 2V over 20 sec

$$\cancel{I_{avg}} \quad I_{avg} = \frac{\Delta Q}{\Delta t}$$

$$\Delta Q = CV = .5F \cdot 2V = 1C$$
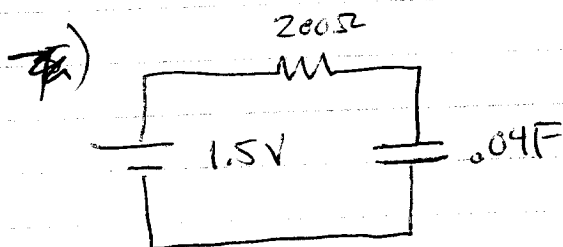
$$I_{avg} = \frac{1C}{20 \text{ sec}} = \boxed{.05A}$$



a) V/R is the initial charging current (when $V_c = 0$).

Since final charge is never achieved (takes infinite


time), then average charging current is zero! So, this is as plausible a

"typical" current as any. $\frac{V}{R} = \frac{1.5V}{200\Omega} = \boxed{.0075A}$


b) $Q_{final} = CV = .04F \cdot 1.5V = .06C$

$$I_{typ} = \frac{\Delta Q}{\Delta t} \Rightarrow \Delta t = \frac{\Delta Q}{I_{typ}} = \frac{.06C}{.0075A} = 8 \text{ sec}$$

c) $I_{typ} = \frac{V}{R} \Rightarrow \Delta t = \frac{Q}{I_{typ}} = \frac{CV}{V/R} = \boxed{RC}$ (no V dependence)

 This is the same as τ - the characteristic time!

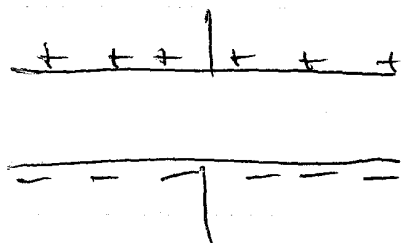84) We always store equal and opposite charges on the opposing plates — $+Q$ on one & $-Q$ on the other. So this



always tends to pull the plates together.

In fact, the capacitor never stores any net charge, simply separates the $+$ and $-$ charges slightly.