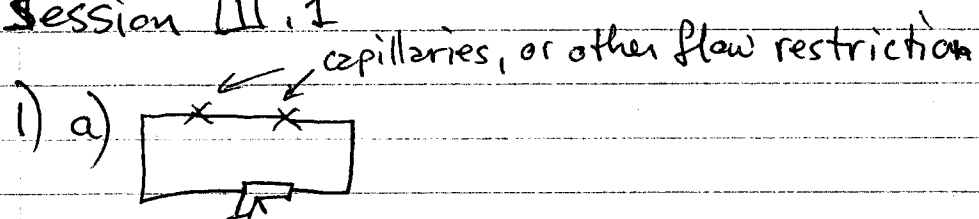


# Physics 132 HW III


## Session III.1



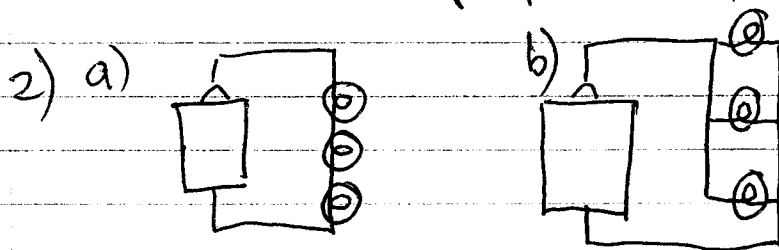b) If a constant flow source, then same flow through 2 in series as for a single bulb, since same current flows through each bulb, and total flow is unchanging.


If a constant pressure source, then less

flow through 2 in series than for single bulb. Pressure drops across each capillary/bulb must add up to total pressure pump supplies, which is a constant. So  $\Delta P$  across an individual bulb ~~also~~ decreases when a second bulb is added, and current therefore decreases proportionally.



c) Type a) is cheaper—since only one wire goes from one bulb to the next.


## Session III.2

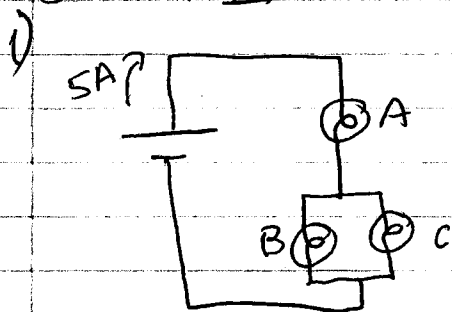


All of current goes through A (5A)

Current is split evenly between B & C (2.5A each)

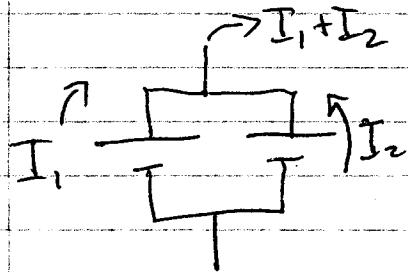- 2) If I have two constant current sources, & I want currents to add they must be combined in parallel:



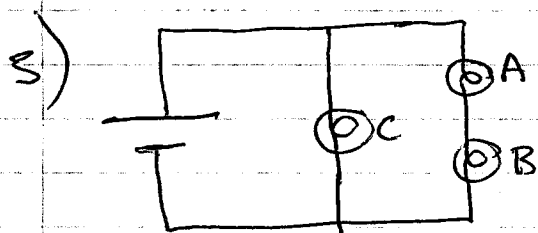Otherwise, in series, best possible result is greatest of  $I_1$  &  $I_2$ , & more likely some value in between



a)  $\Delta V$  across C is  $V_{\text{batt}}$

$\Delta V$  across A +  $\Delta V$  across B =  $V_{\text{batt}}$

so  $C > A = B$

↑ since identical & in series


- b) A single bulb would have  $\Delta V = V_{\text{batt}}$ , which is = C. A & B dim relative to this.

### Session III.3

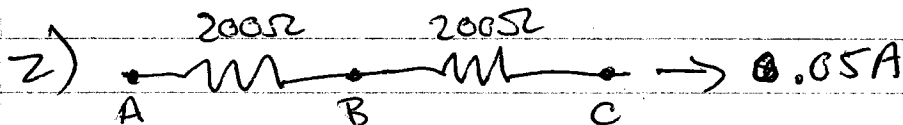1)  $200\Omega = R$   $I = 50\text{mA} = .05\text{A}$

$\Delta V = ?$


$\Delta V = IR = .05\text{A} \times 200\Omega = 10\text{V}$



a)  $\Delta V_1 = V_B - V_A = IR = 10\text{V}$

b)  $\Delta V_2 = V_C - V_B = IR = 10\text{V}$ , so  $\Delta V_{\text{total}} = V_C - V_A = \Delta V_1 + \Delta V_2 = 20\text{V}$

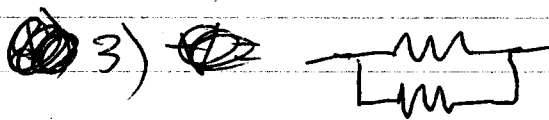c)  $\frac{\Delta V_{\text{tot}}}{I} = \frac{20\text{V}}{.05\text{A}} = 400\Omega$




$\Delta V = \text{same as original} = 10\text{V}$

a)  $I_2 = \frac{\Delta V}{R} = .05\text{A}$

b)  $I_{\text{tot}} = I_1 + I_2 = .1\text{A}$   $R = \frac{\Delta V}{I} = \frac{10\text{V}}{.1\text{A}} = 100\Omega$


In general, 2 identical R's in parallel  $\rightarrow R_{\text{eff}} = \frac{R}{2}$

c) Twice area is like

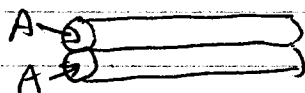

which is  $\frac{R}{2}$

or

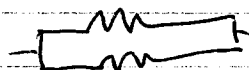

### Session III.3

3d)  $R = \frac{\rho l}{A}$

For Cu wire,  $\rho = 1.7 \times 10^{-8} \Omega \cdot \text{m}$

We assume diam = 1 mm, so  $r = .0005 \text{ m}$

and  $A = \pi r^2 = 7.85 \times 10^{-7} \text{ m}^2$

$l = 30 \text{ m}$ , so

$$R = \frac{1.7 \times 10^{-8} \Omega \cdot \text{m} \cdot 30 \text{ m}}{7.8 \times 10^{-7} \text{ m}^2} = .65 \Omega$$